

# Advanced Concepts for Fusion Power Supplies



Dr. Jin Wang

Department of Electrical and Computer Engineering


wang@ece.osu.edu  
614-688-4041

June 37 2011

# Challenges and Opportunities in Fusion Power Supplies
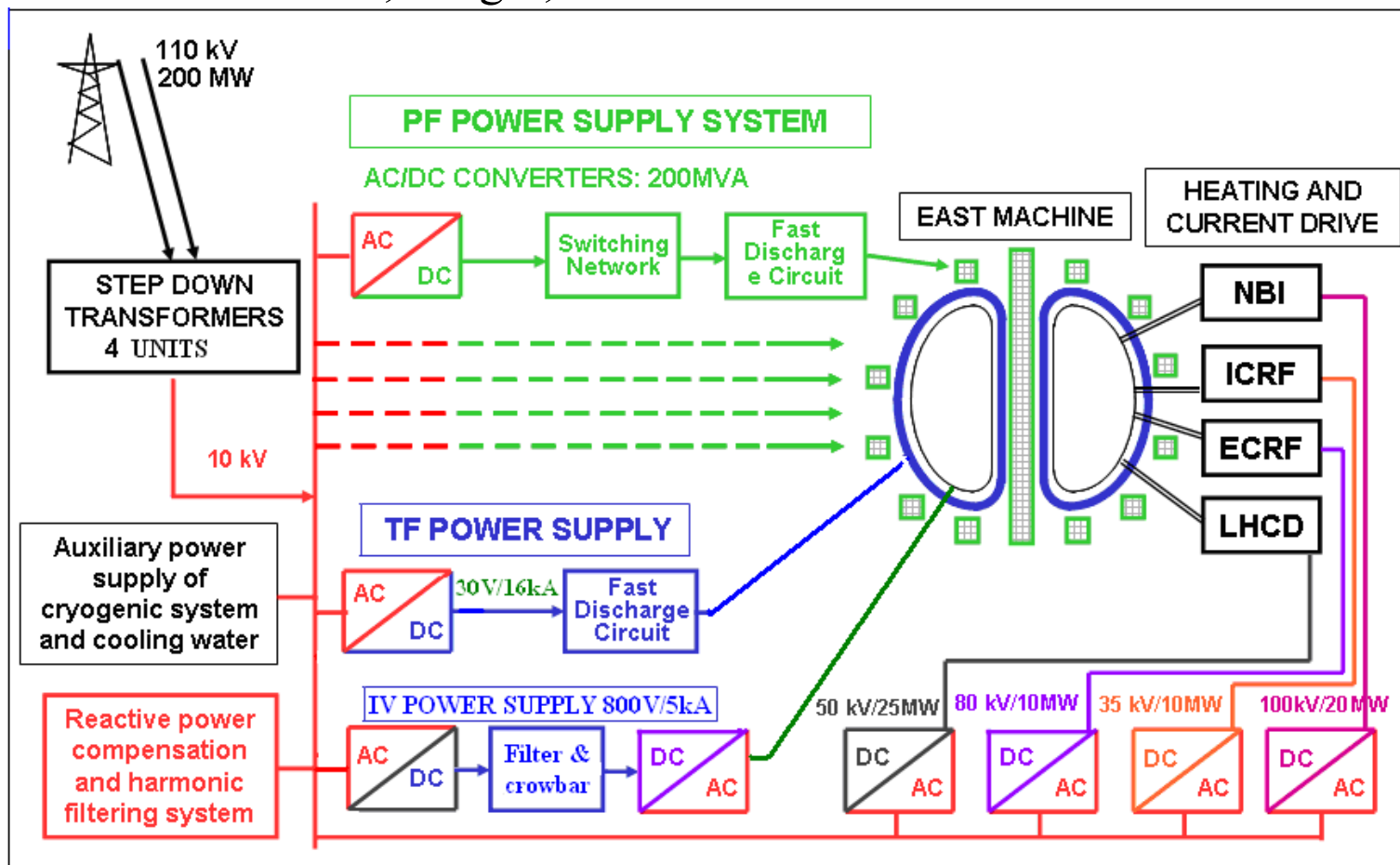
## Extremely sophisticated high voltage power electronics network

- Large numbers of conversion units;
- Dynamic response required by new functions;
- Reactive power and harmonics issues;
- Size, weight, and cost.



System  
Diagram of  
the EAST  
Tokamak

Picture courtesy:  
Institute of Plasma  
Physics, China

## **Opportunity for optimizations overall power supply systems**

- Universal modular circuits
- Control coordination between each function blocks

## **Newer and emerging technologies in power electronics**

- IGBT and IGCT based switching circuits
- Multilevel inverters/converters
- Switched capacitor circuits
- Wide band gap devices, such as SiC and GaN

## **Modular circuit structures**

- Lower voltage/current stress for individual switching devices
- Lower costs
- Better power quality
- Fail safe

## **Adaptation of wide band gap devices**

- Better efficiency
- Smaller footprint and weight
- Better dynamic response


## **Distributed real time simulation**

- Hardware-in-the-loop based algorithm development
- Platform for system level coordination and optimization

**Modular Circuit Structure Example: M<sup>2</sup>LC for  
Vertical Stabilization (VS) coils**

# Modular Circuit Structure Example: M<sup>2</sup>LC for Vertical Stabilization (VS) coils

## Modular Multilevel Converter

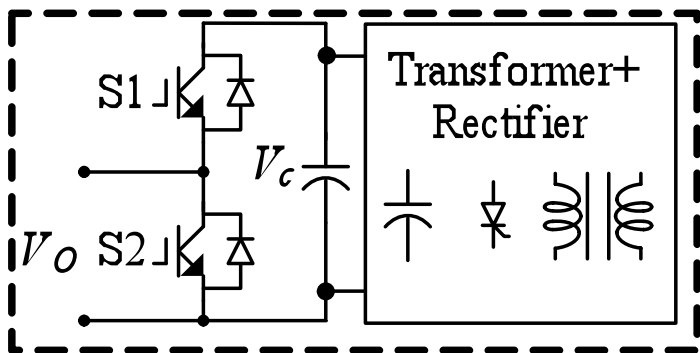


Basic switching module

Switching status	S1	S2	$V_o$
1	On	Off	$V_c$
2	Off	On	0


Active switching status

$$V_o = \frac{1}{2} V_c + \frac{1}{2} V_c \cdot M \cdot \sin(\omega t)$$

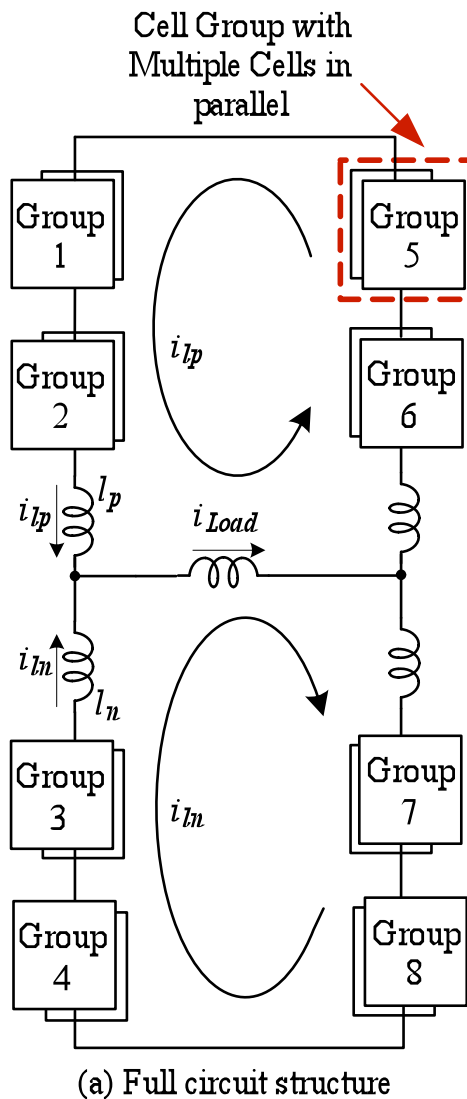
## Equivalent output at pure sinusoidal Pulse Width Modulation



(a) Full circuit structure

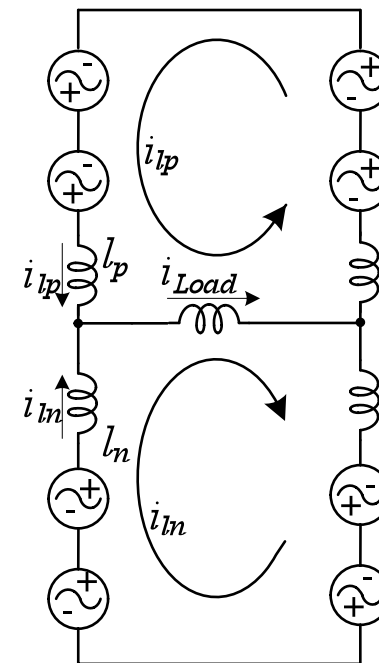

(b) Equivalent ac model

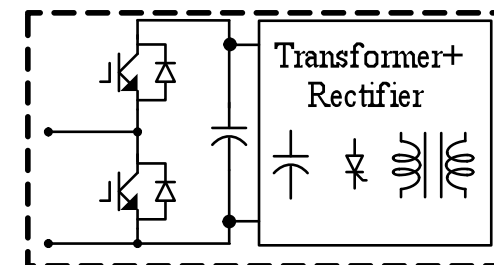


(c) Single cell structure

# Control Strategy


## Control Goal:

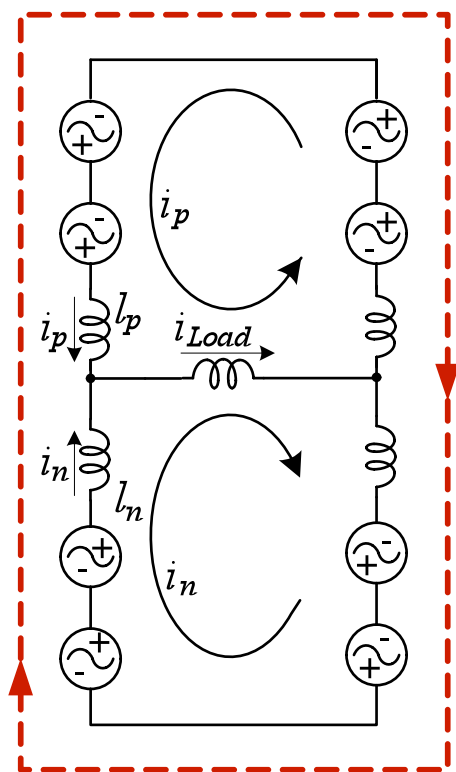1. Regulate the VS coil current
2. Minimize looping current



## Control Strategies

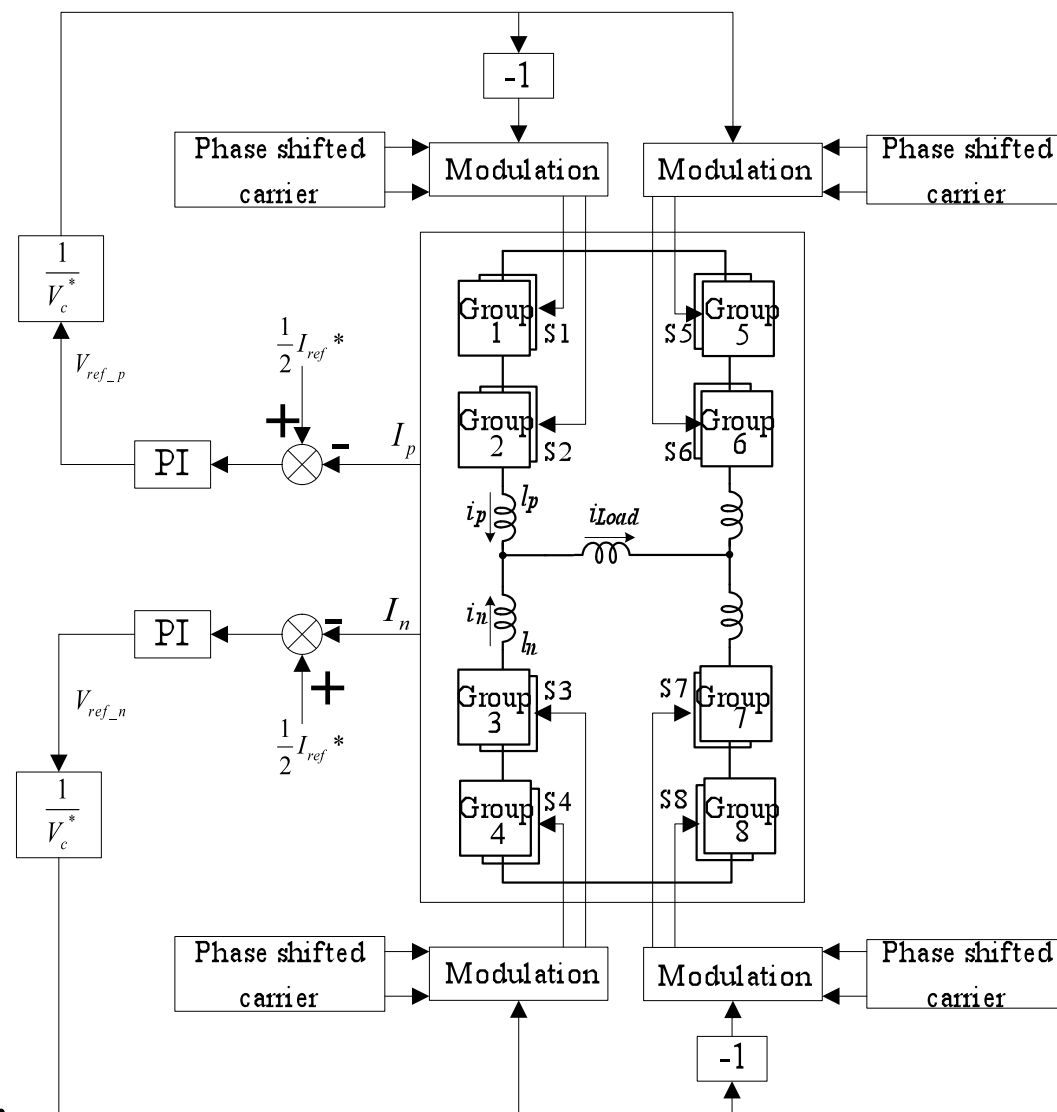1. Independent control of  $i_p$  and  $i_n$
2. Multi-carried phase-shifted Pulse Width Modulation





## Simulation of the M<sup>2</sup>LC for a VS coil

Load inductance L	1.4 mH
Load resistance R	10 m
Buffer inductance $L_p, L_n$	5 uH
Module capacitance	2 F
Capacitor voltage in cell groups 1&2 ( $V_{lu}$ )	1185 V
Capacitor voltage in cell groups 3&4 ( $V_{ll}$ )	1200 V
Capacitor voltage in cell groups 5&6 ( $V_{ru}$ )	1230 V
Capacitor voltage in cell groups 7&8 ( $V_{rl}$ )	1170 V
Carrier frequency	2 kHz
Proportional gain Kp	5 V/A
Integral gain Ki	10V/(A s)



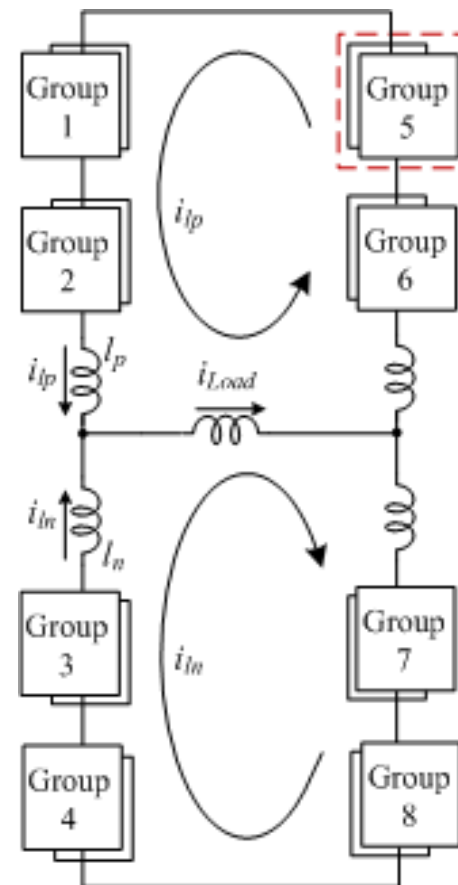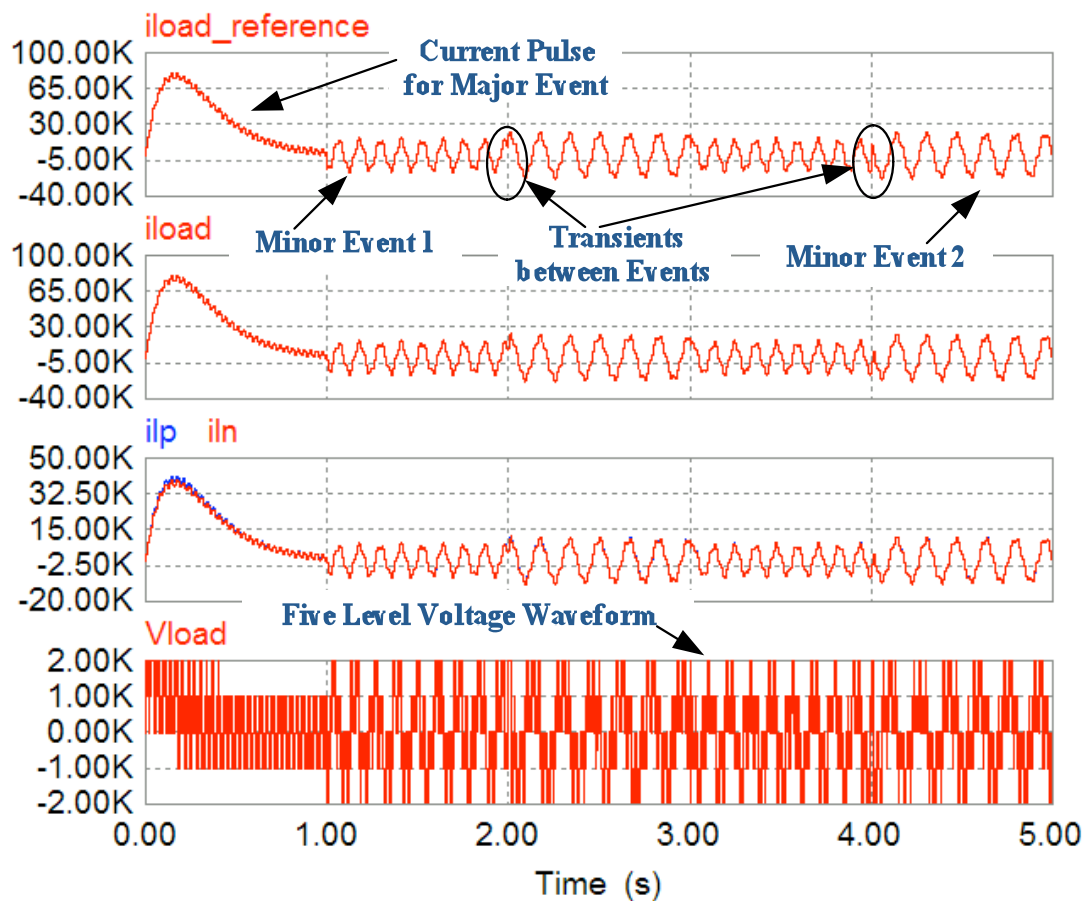
## Simulation Results: M<sup>2</sup>LC for Vertical Stabilization (VS) coils




The current reference has one major event and two minor events. A continuous 30 Hz 3000 Ampere “noise” is added on top of all the events.

## By-pass Operation of Faulty Modules, Case I

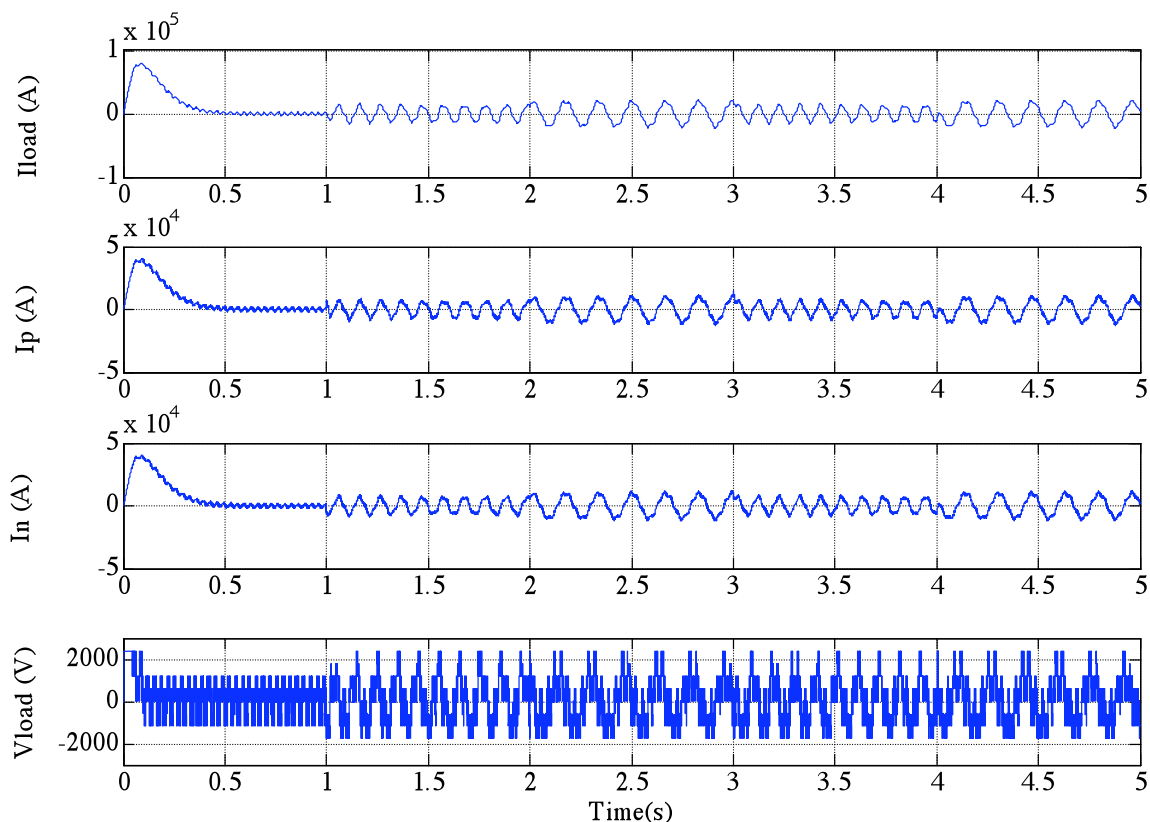

**At 2.5 s, assuming there was a device failure, Group 1 was shorted out.**

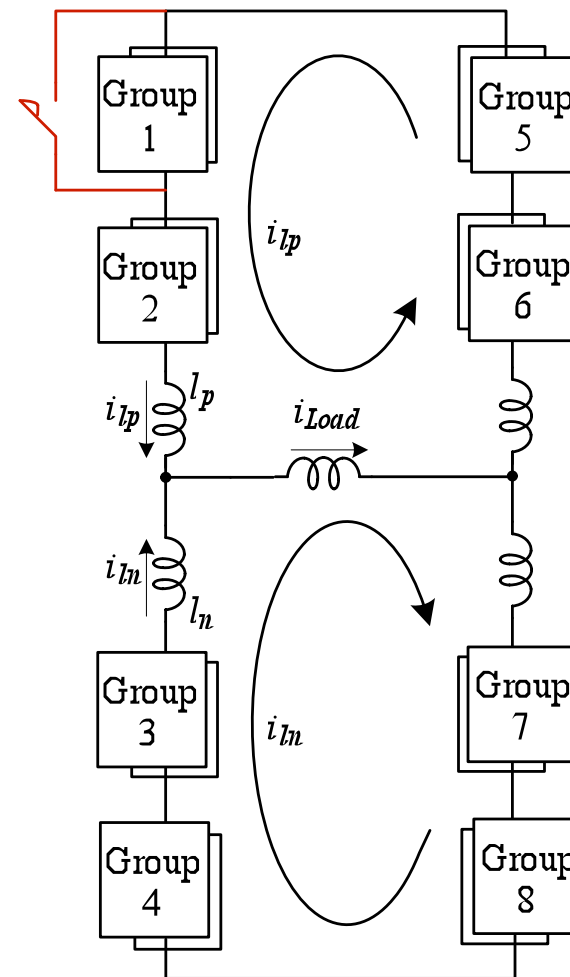**Because of the robust control strategy and redundant voltage for the two minor events, the load current is not affected.**



## Advantages of the Circuit


---

- ❑ **lower voltage stress on switching devices;** with lower voltage stresses, 1400 V to 1700 V rated IGBTs could be used; usually, IGBTs at this voltage range can be switched at a higher frequency than IGCTs; thus, superior dynamic response could be achieved;
- ❑ **lower current stresses;** since  $i_{load}$  is the summation of  $i_{ln}$  and  $i_{lp}$ , each cell (cell group) only needs to supply half of the load current;
- ❑ **expandability;** if needed, more cell (cell groups) can be connected in series to achieve a higher voltage level;
- ❑ **multiple level output;** high resolution current control with low switching frequency and good efficiency;
- ❑ **fail safe;** failed module could be disconnected while the full system goes through safe shut down process.

# **Adaptation of Wide Band Gap Devices**

## Adaptation of Wide Band Gap Devices


### Roadmap of major device manufactures

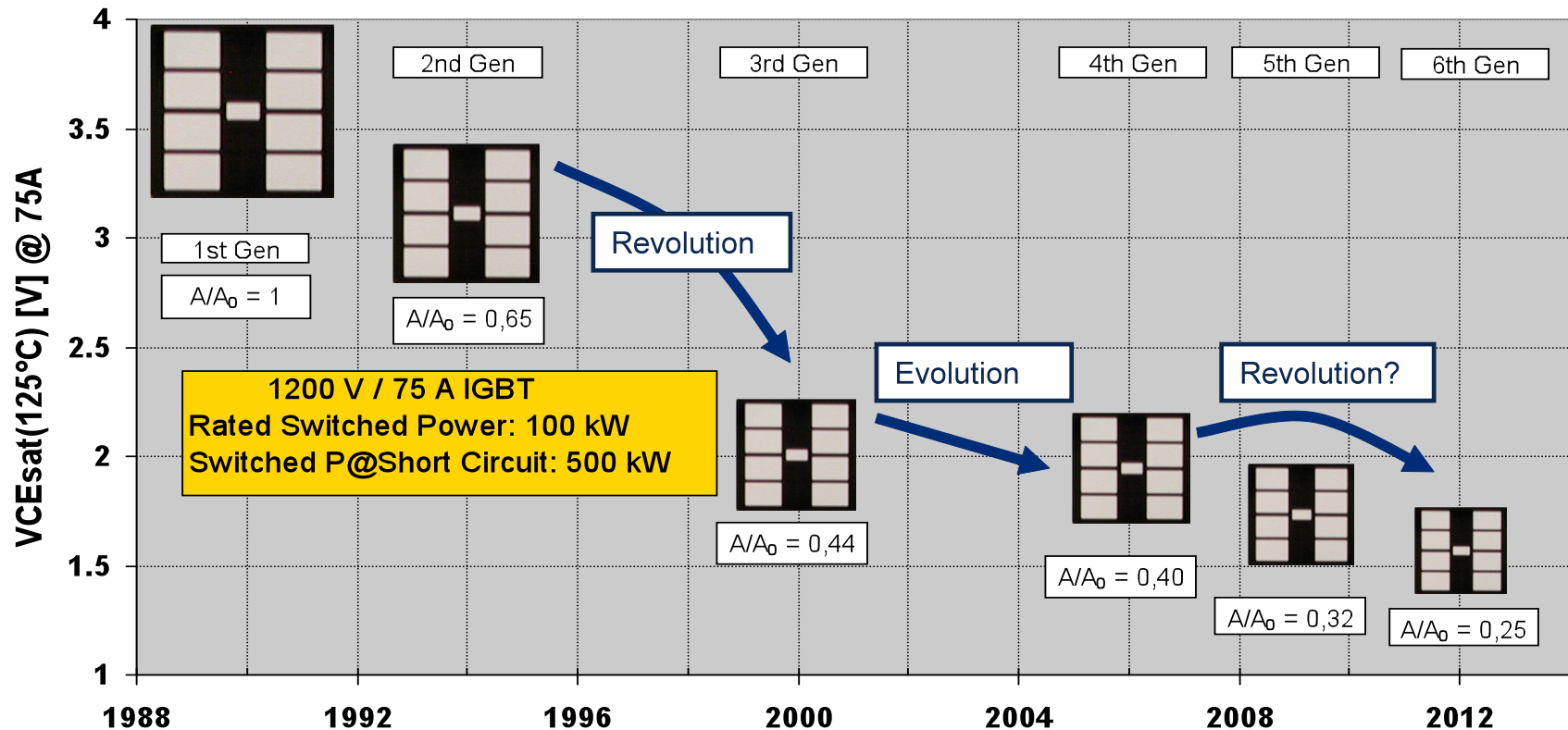

*Infineon*: High Temperature Power Electronic Devices and Packaging for HEV

- Development of Si based chips for power switching has come to an end.
- The two development directions are: better cooling strategy and wide band gap devices.

## On Resistance vs. Breakdown Voltage

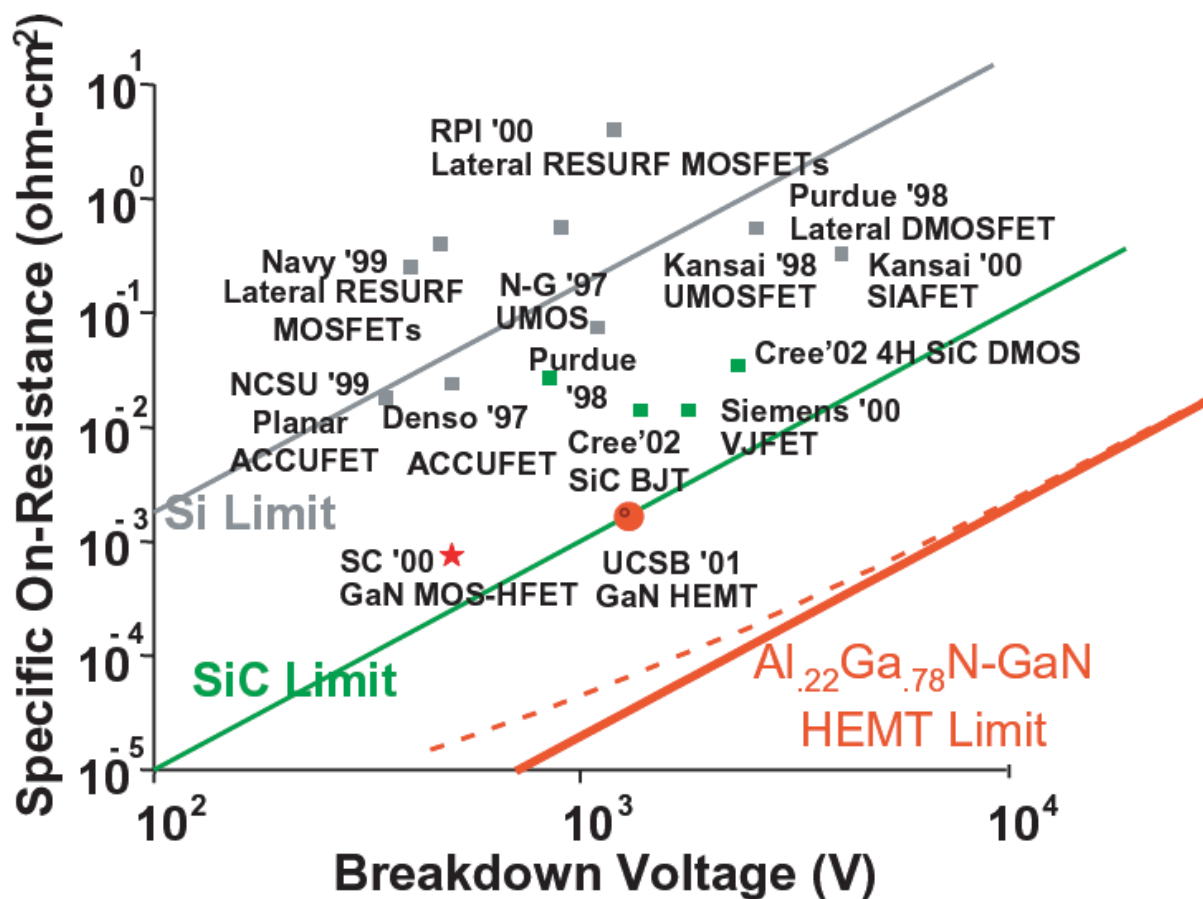


SiC have 10X lower total power dissipation than Si.


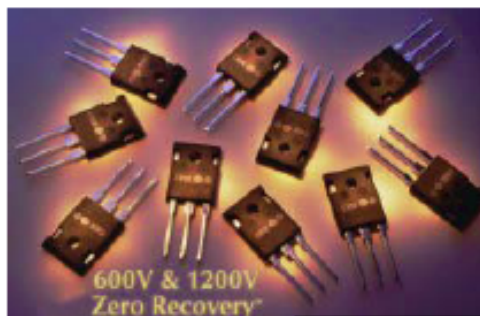
## SiC Power Devices Commercial Availability




- Silicon Carbide Schottky rectifiers commercially available from 3 sources:
  - CREE, Inc (NC), SiCED (Siemens/Infineon-Germany), SemiSouth Laboratories (MS)



Product links to U.S. Manufacturers Diode Products

<http://www.semisouth.com/products/powersemi.html>


[http://www.cree.com/products/power\\_docs2.asp](http://www.cree.com/products/power_docs2.asp)

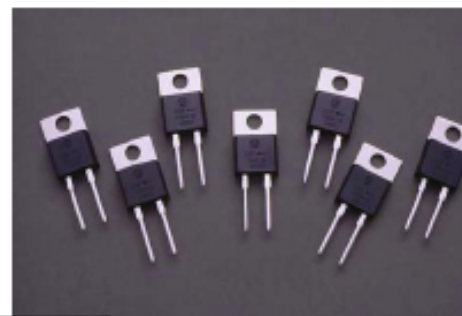

TRL 9

11 x 10<sup>6</sup> Amps  
Delivered in 3Q 2008  
Commercial viability an implied requirement for DoD availability.


COST  
RELIABILITY  
PERFORMANCE

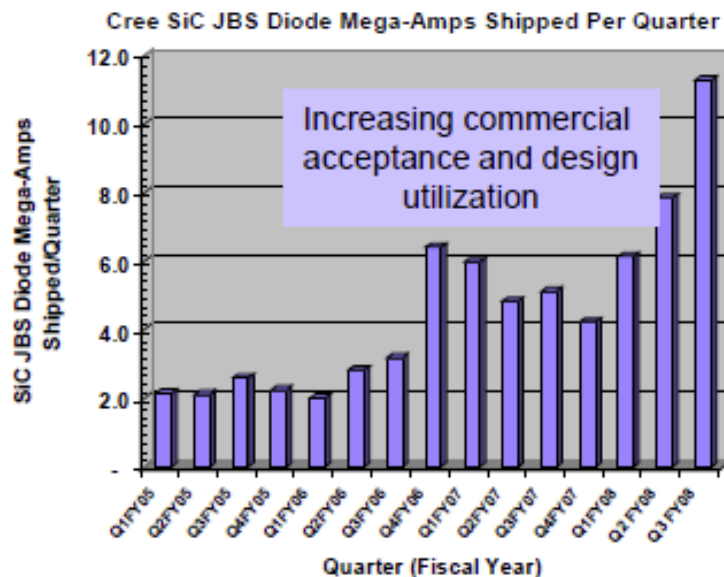


- Over 2x Price Reduction
1. Higher Quality SiC Material
  2. Larger Production Volumes
  3. Increase SiC Wafer Size from 3 inch to 100 mm

Lack of a switching product slowed large scale adoption

## Megawatt scale applications

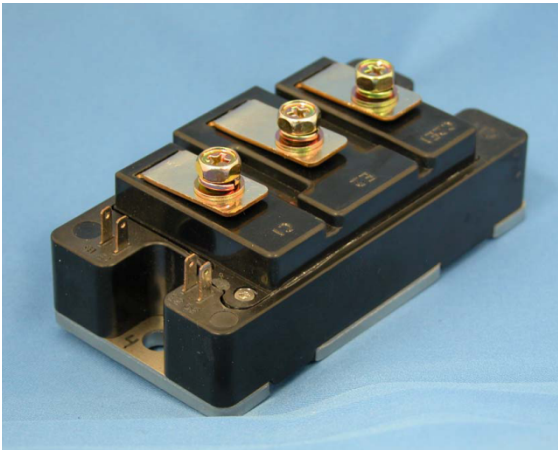

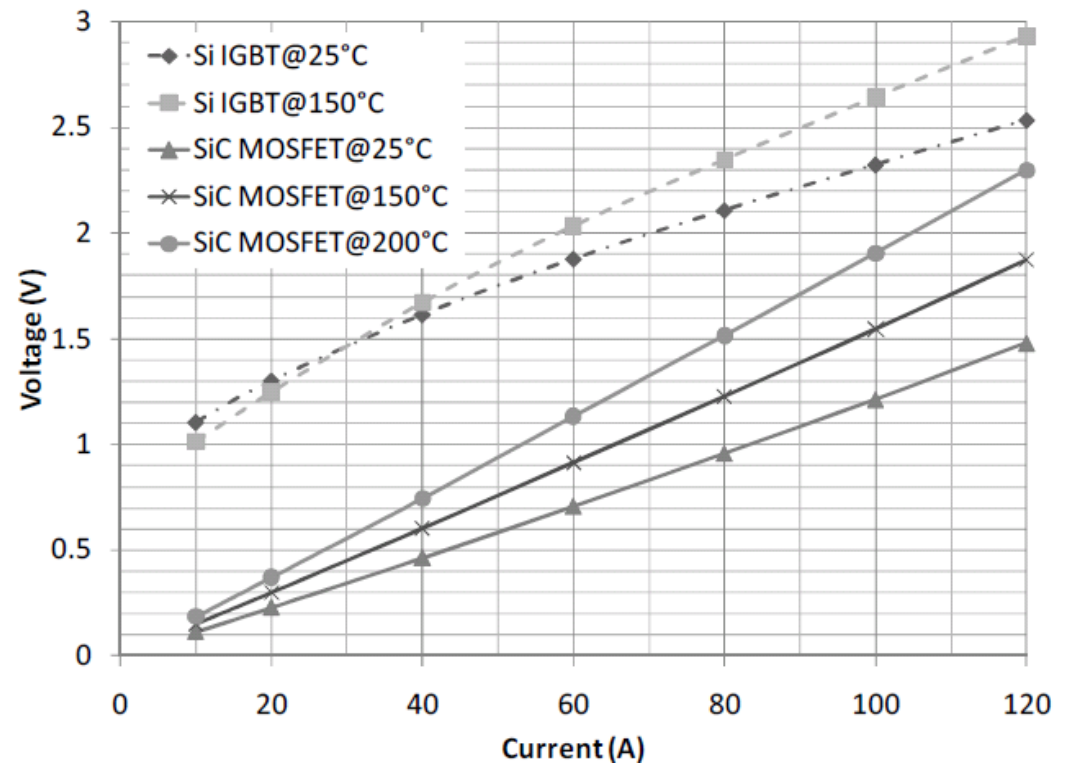External view of 1.2kV/100A, all-SiC Half H-Bridge power module



Comparison of on-state voltage between the 1.2kV/100A SiC module and the equivalently rated Si IGBT module (CM100DY-24NF)

Jim Richmond, Scott Leslie, etc. "Roadmap for Megawatt Class Power Switch Modules Utilizing Large Area Silicon Carbide MOSFETs and JBS Diodes"




## High Voltage Devices

9% Weight and 12% Volume vs IGBT module




High Voltage Silicon Carbide Power Devices. [Online]. Available: <http://arpa.e.energy.gov/LinkClick.aspx?fileticket=RaTsvSs0acE%3D&tabid=116>
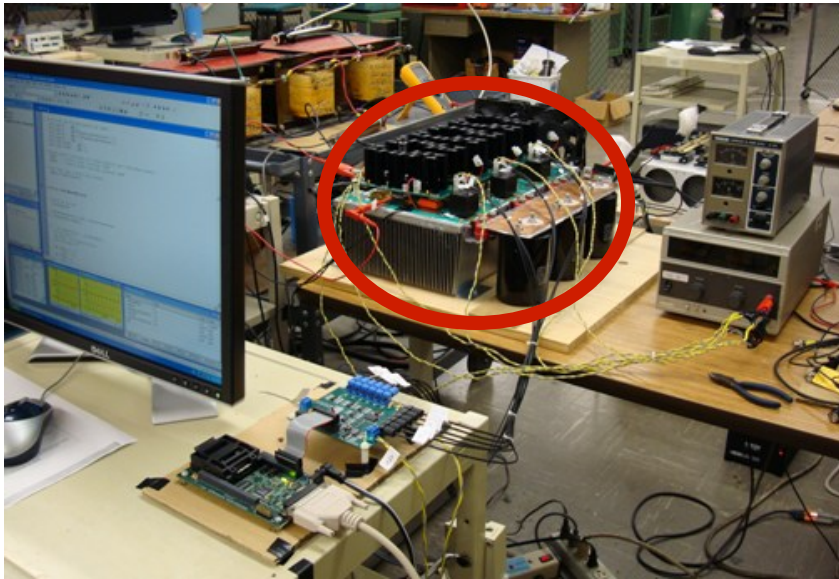
# OSU 30 kW SiC JFET Inverter and GaN Tests



**30 kW SiC JFET Inverter**

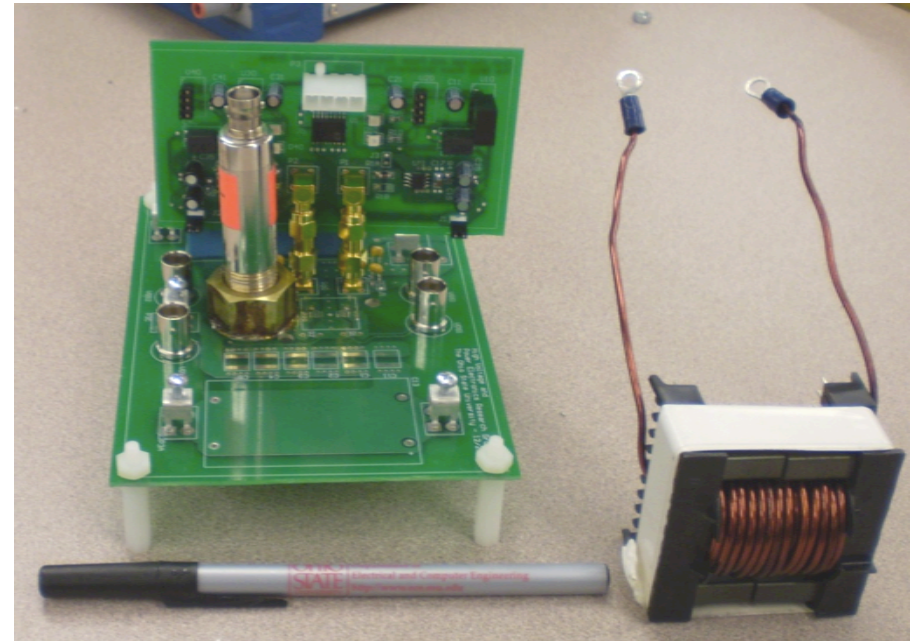


**GaN Test Board**

# **Distributed Real-time Simulation**


## Real-time simulation for Electric Power Systems

**Real-time Simulation** refers to a computer model of a physical system that can execute at the same rate as actual "wall clock" time. In other words, the computer model runs at the same rate as the actual physical system.


### Model of electric power systems

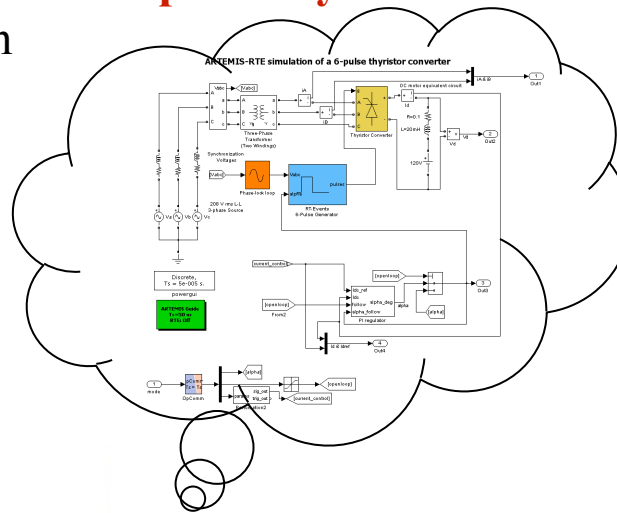

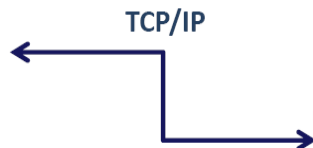- 4 real-time target machines;
- 10 CPUs;
- PCI links between targets;
- 512 Digital I/O;
- 4 Xilinx FPGAs
- 282 Analogue I/O.




**I/O and real-time model execution**

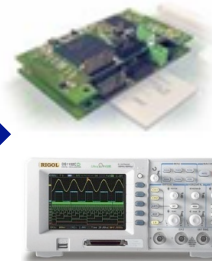

**External monitoring and control units**


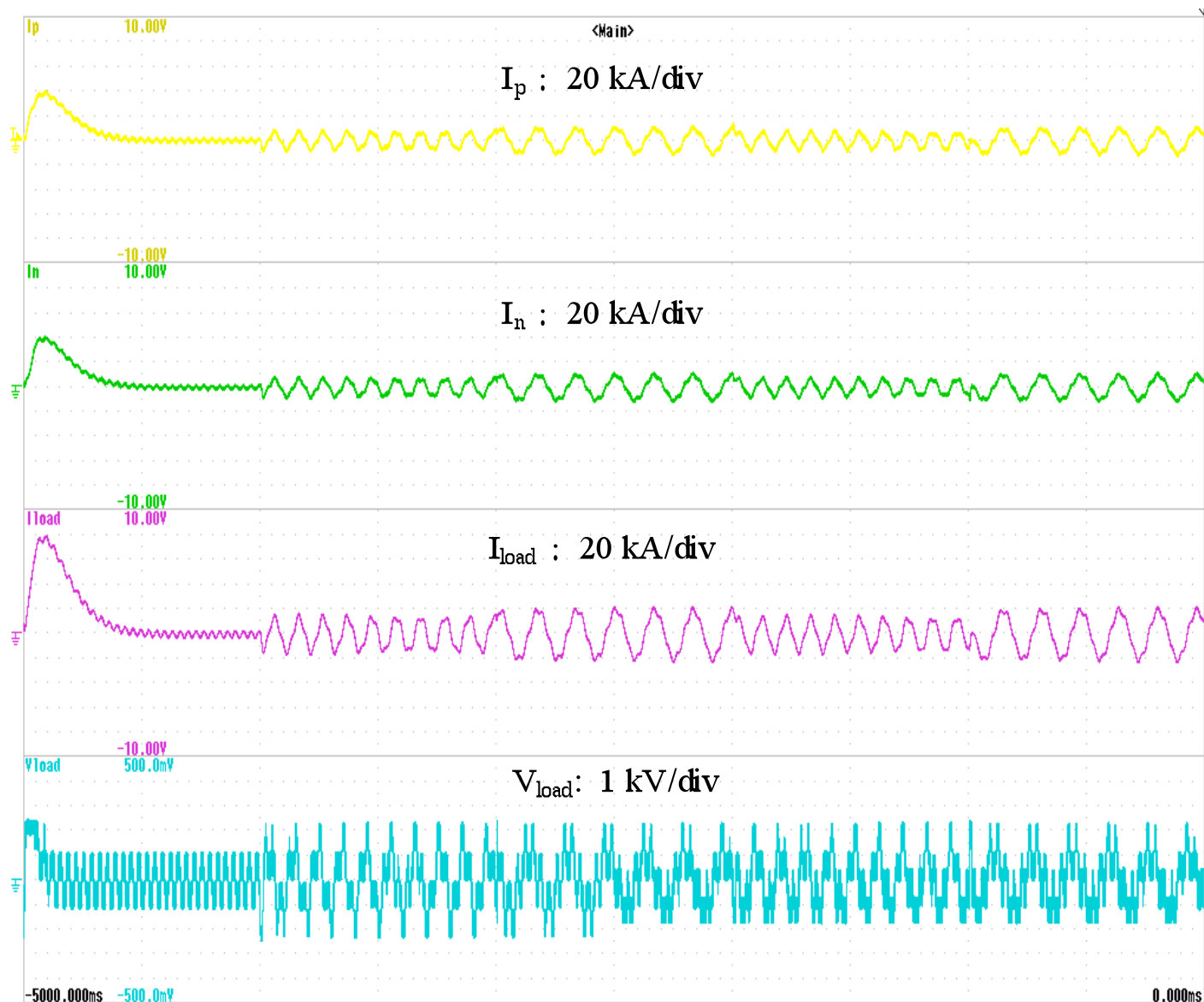
# Real Time Simulation Results of the M<sup>2</sup>LC for a VS coil



Simulation Results Observed with Digital Oscilloscope (Yokogawa DL480V)
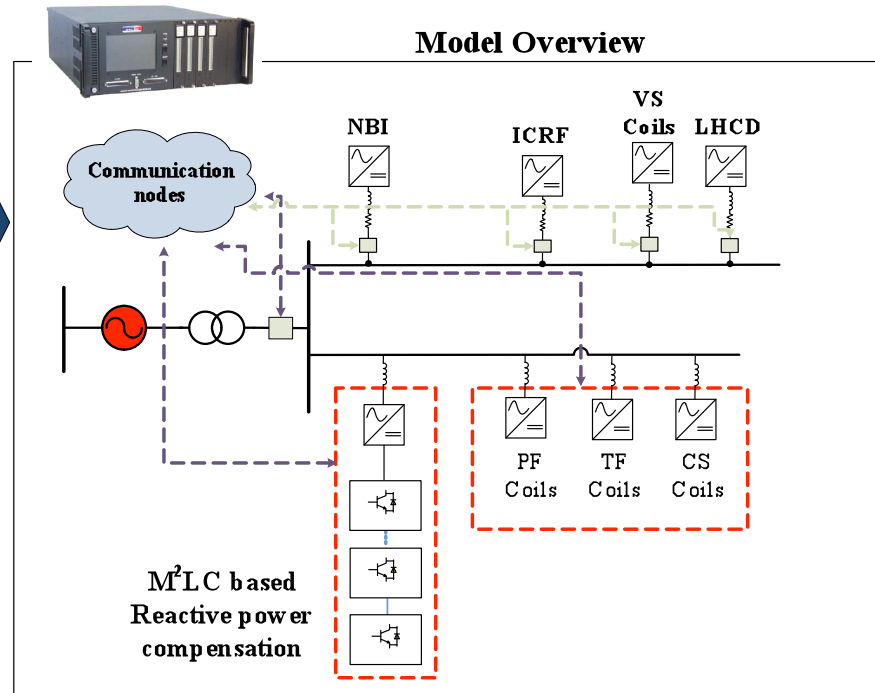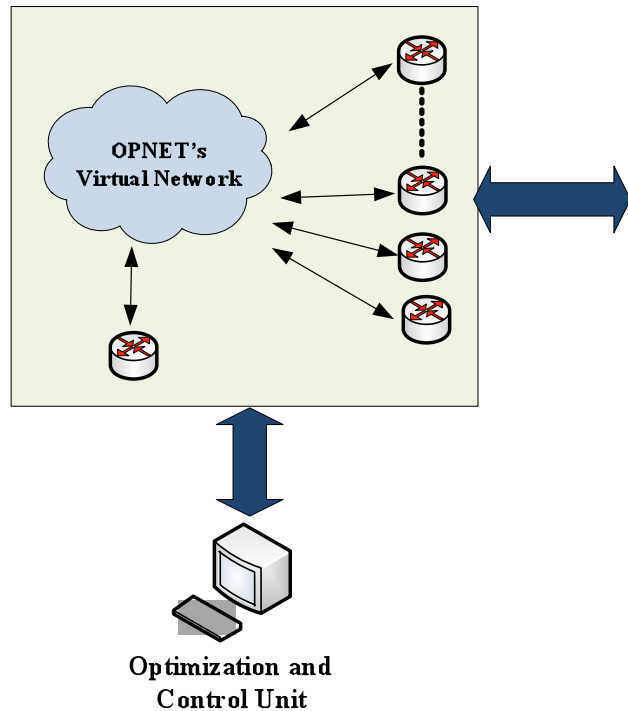
# Next Step: System-in-the-loop based Real Time Simulation and Analysis

Real time simulation of Communication Network



Real time simulation of Electric Power System

- Combine real time simulations of electric power system and real time simulation simulations of communication (system-in-the-loop) network;
- Analysis the impact from communication network failure and latency;
- Pave the road for system level coordination/optimization.

*Thanks Questions attention.*